

scientific  
analog

# Modeling Digital PLL Components in *XMODEL*


---

Scientific Analog, Inc.

July 2017

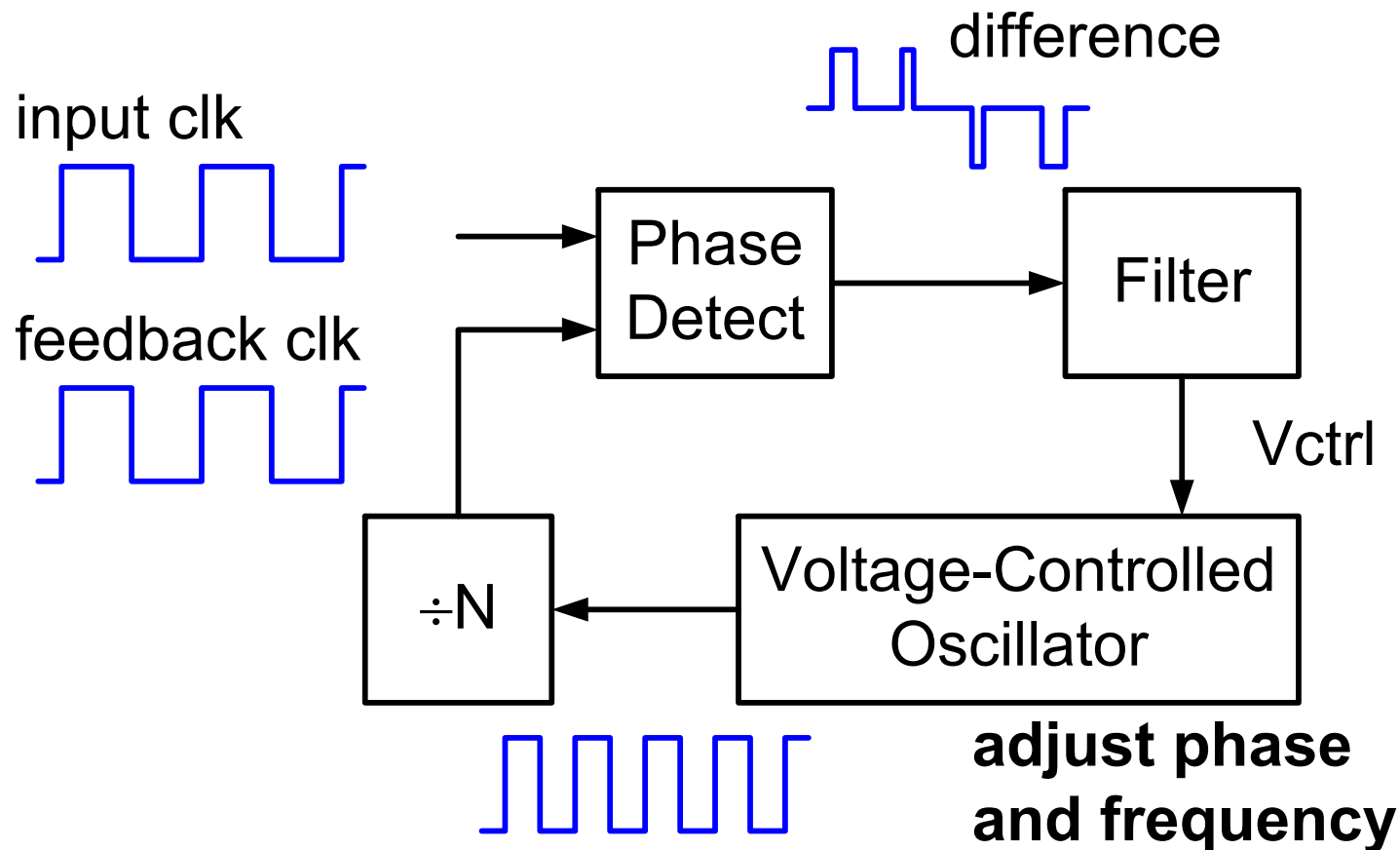
# Phase-Locked Loop (PLL)

- PLL is a system that aligns its output clock to the input clock via feedback



 
# Synchronize Two Clocks

- Charlie and Lucy want to meet at 6 o' clock sharp everyday
- But their watches have
  - phase offset
  - frequency offset
- Only Lucy can adjust Charlie's watch when they meet



 
## Lucy's 1st Idea

- Adjust Charlie's watch so that it points the same time with Lucy's
- Hoping that they will stay synchronized till tomorrow
- Will it work?



 
# Frequency Offset Causes Phase Drift

- If Charlie's clock doesn't tick at the same rate with Lucy's, his clock will always be off after a day
- Lucy realizes time error has two components
  - phase error
  - frequency error



 
## Lucy's 2nd Idea

- Cancel the phase drift in advance
  - so the clocks will be synchronized the next day
- But Lucy must know the drifting rate (freq. offset)
  - Estimate it based on the past time differences
  - while fixing phase offsets



# That's What a PLL Does

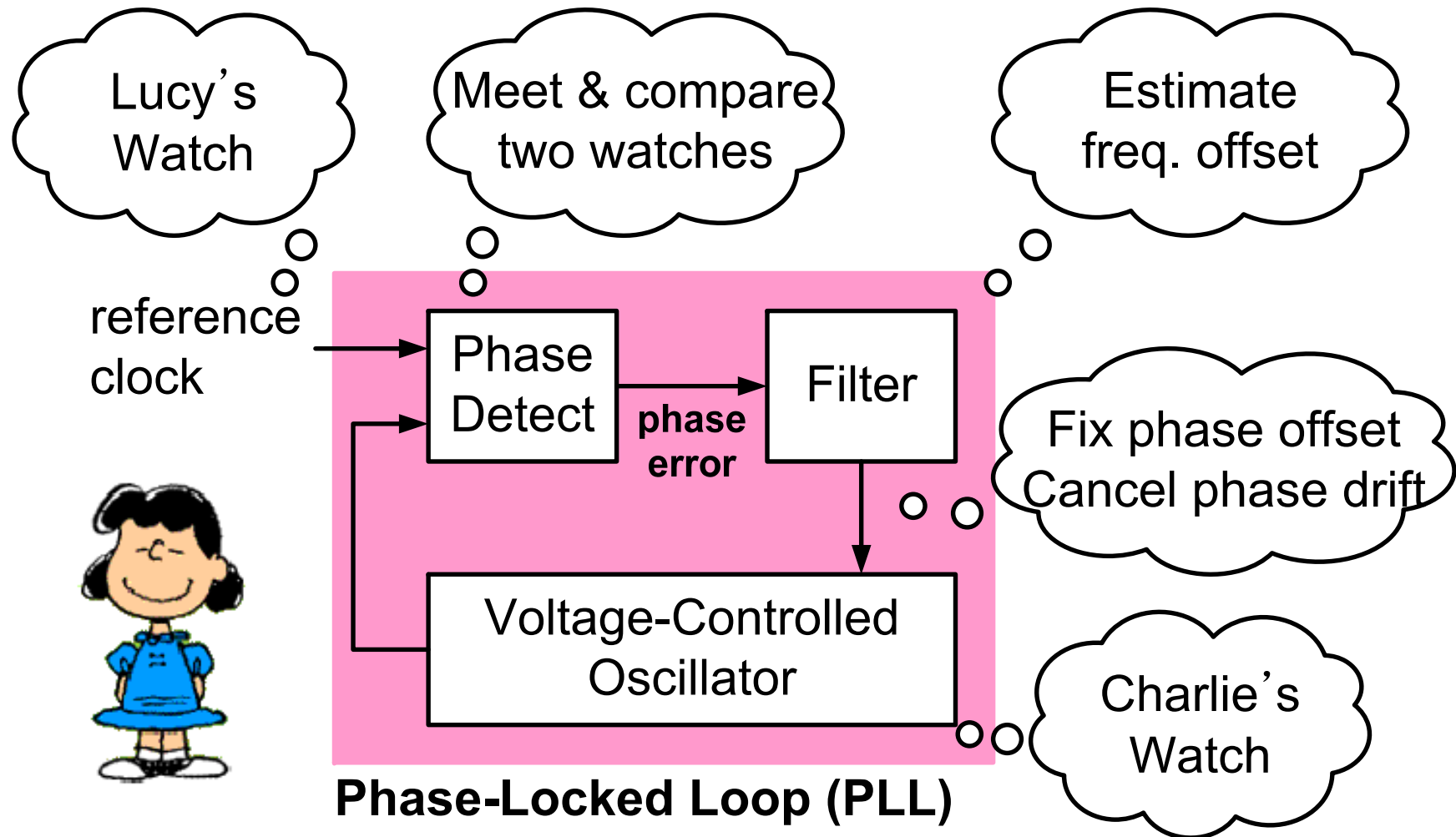


# PLL Control Basics

- Goal is to make the reference phase ( $\phi_{\text{ref}}$ ) and feedback phase ( $\phi_{\text{fb}}$ ) the same
  - Make Lucy and Charlie arrive at the same time
- Upon the detection of the phase error ( $\phi_{\text{err}}$ ), the PLL adjusts two things from the output clock:
  - The phase:  $\phi_{\text{out}} \leftarrow \phi_{\text{out}} + K_1 \cdot \phi_{\text{err}}$   
(The current time of Charlie's watch)
  - The frequency:  $\omega_{\text{out}} \leftarrow \omega_{\text{out}} + K_2 \cdot \phi_{\text{err}}$   
(The current estimate of Charlie's watch tick rate)
- There are two variables that Lucy needs to control – a second-order system!






# Charge-Pump PLL

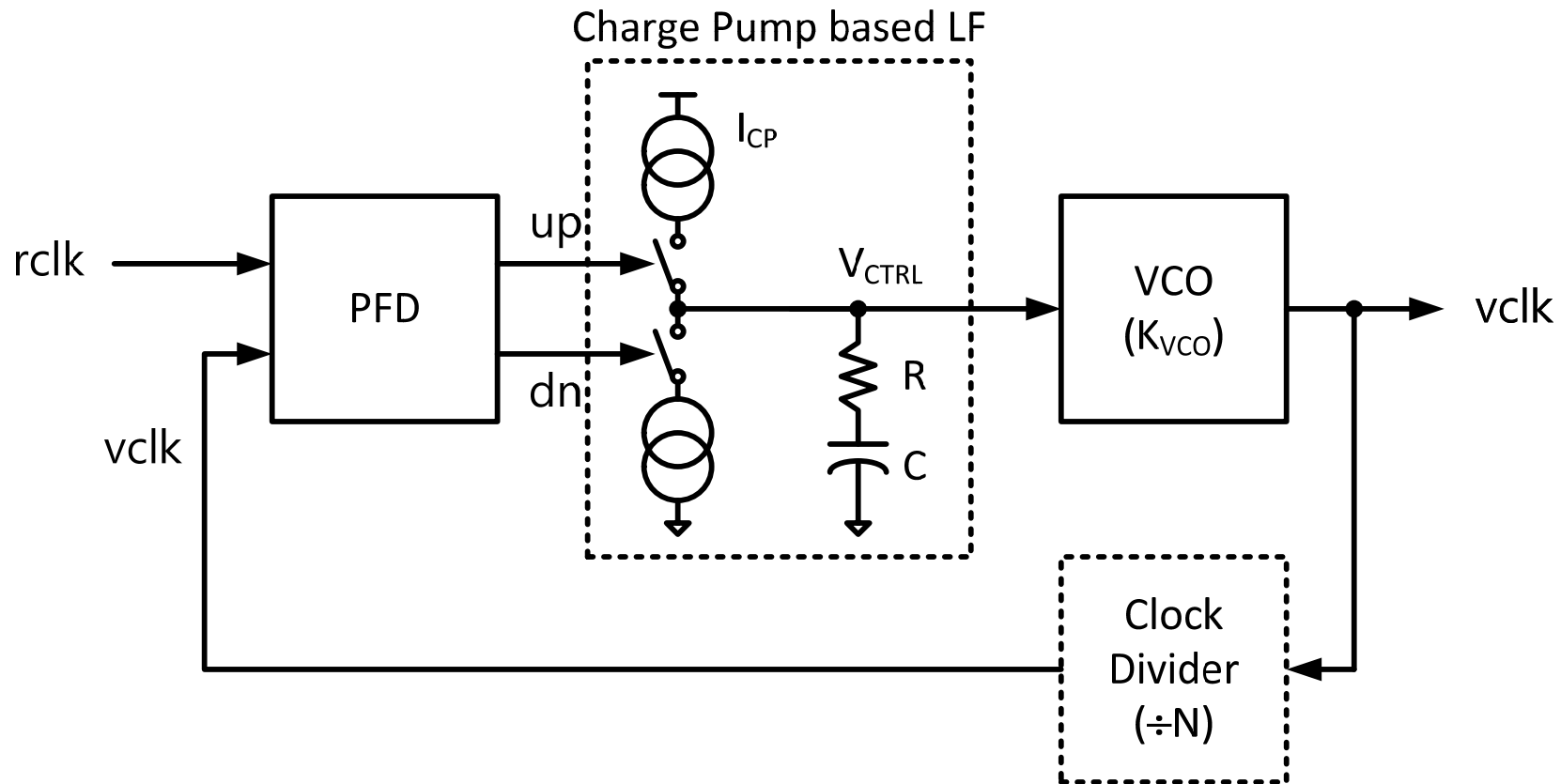

- Uses a charge pump followed by an RC filter as the loop filter (controller)

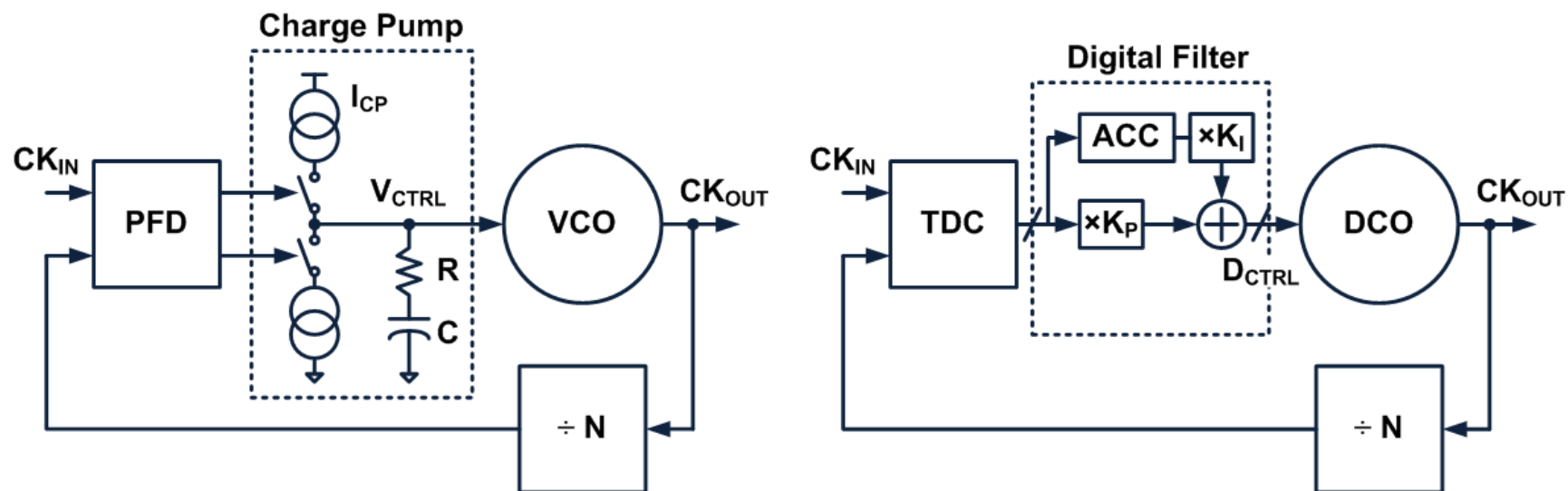
# Digital PLLs

- Use accumulators instead of charge pumps to:
  - Overcome technology limitations such as CP current mismatch, capacitor leakage, design difficulty, etc.
  - Implement transfer functions, calibrations, fast-settling algorithms that are difficult with analog


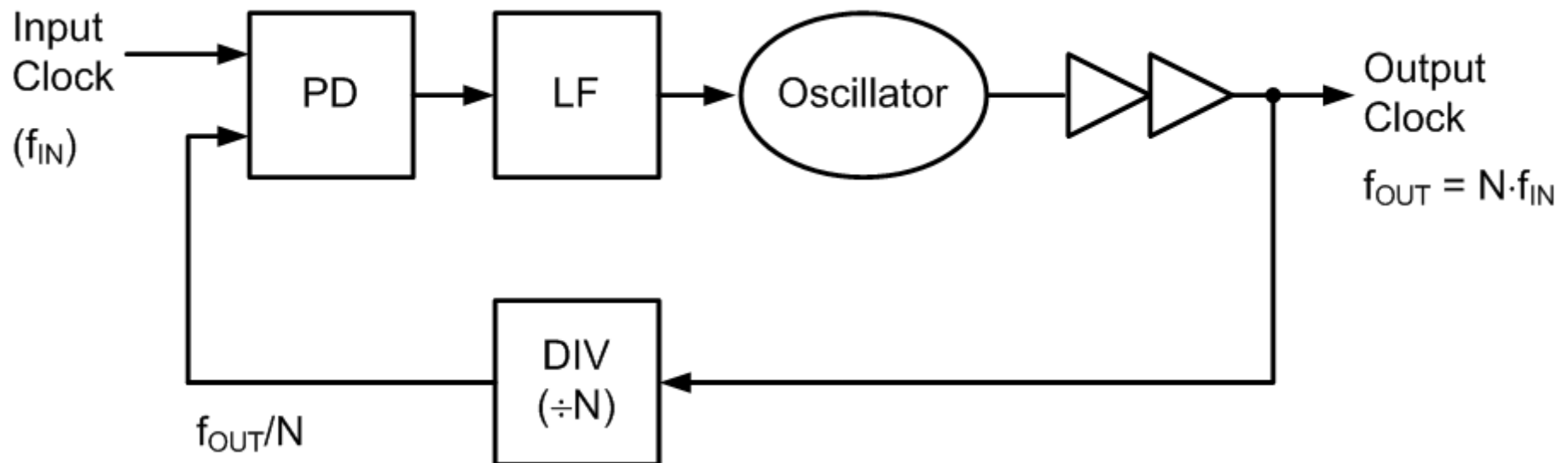
# Frequency Multiplication with PLL

- By inserting a divider ( $/N$ ), the PLL will lock when the output frequency is  $N$  times the input frequency




# PLL Components

---

- Just with any feedback loop, a PLL comprises of:
- **Producer (DCO):** generates the output clock with desired phase/frequency
- **Sensor (TDC):** measures the error between the output and the reference input
- **Loop filter or Controller:** decides how to adjust the control input of the producer based on the measured error
 
# Time-to-Digital Converter (TDC)

- Converts the timing difference between the two input clocks into a digital code
- The ideal TDC can be constructed using the *clk\_to\_delay* and *adc* primitives



# Ideal TDC Model

- models/tdc\_ideal.sv:


```
...
clk_to_delay clk2delay(.trig(clk_ref), .in(clk_fb), .out(delay));

adc    #(.num_bit(4), .value_min(-8*unit_delay),
          .value_lsb(unit_delay))
        delay2dig(.in(delay), .out(dout_xb));

xbit_to_bit    #(.width(4)) conn(.in(dout_xb), .out(dout));
assign out = dout - 4'b1000;
...
```
 
# Exercise: TDC Simulation


- Run the testbench in sim/tb\_tdc\_ideal:



*What are the gain and resolution of this TDC?*
 
# Oversampling TDC

- Digitize the timing difference by oversampling it
  - Multiphase clocks are obtained using a delay line
  - Hence the TDC resolution is set by the buffer delay  $D$





# Oversampling TDC Model

- models/tdc\_dline.sv:

```
// delay line
delay_xbit    #(.delay(0.0))
               delay_fb_0(.in(clk_fb), .out(fbclk[0]));
delay_xbit    #(.delay(unit_delay))
               delay_fb_1(.in(fbclk[0]), .out(fbclk[1]));
...


// phase detectors
dff_xbit      sampler_0(.d(rclk), .q(pd[0]), .clk(fbclk[0]));
dff_xbit      sampler_1(.d(rclk), .q(pd[1]), .clk(fbclk[1]));
...
```

## Exercise

- Finish the encoding logic in tdc\_dline.sv so that the TDC has the same characteristics with the ideal TDC


```
always @(pd_bit) begin
    if (pd_bit == 16'b0000_0000_0000_0000)
        out = 4'b1000;
    else if (pd_bit == 16'b1111_1111_1111_1111)
        out = 4'b0111;
    else
        // fill the logic expression to compute the output here
        out = ...;
end
```

# Results

 

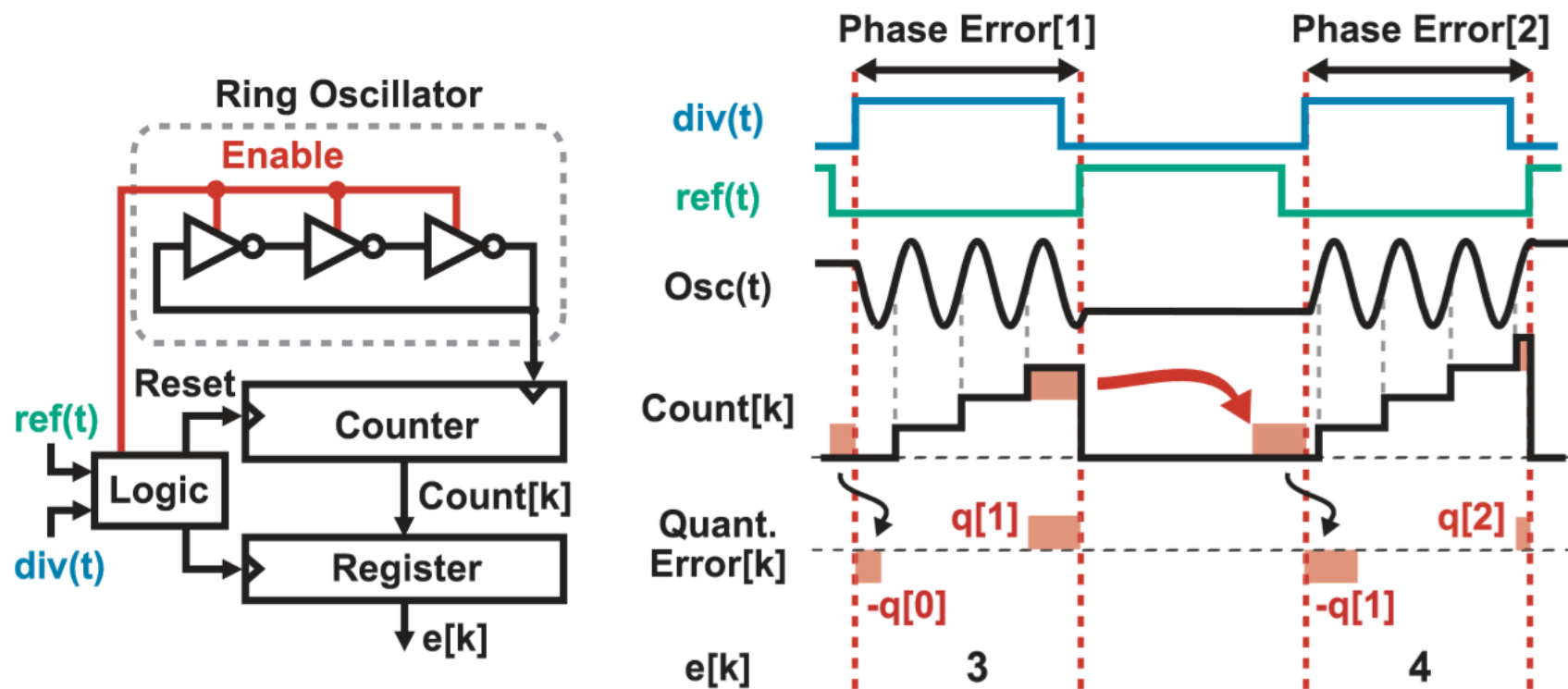
# Gated Oscillator TDC

- Measure the pulsewidth of the PFD output by counting the frequency of the oscillator enabled only while the UP/DN pulse is high [M. Perrott]



 
# Exercise

- Compare the characteristics of all three TDCs
- Run the testbench in sim/tb\_tdc\_all


 
# Digitally-Controlled Oscillator (DCO)

- Produces a clock whose frequency is controlled by a digital input
  - Can be easily modeled using a *freq\_to\_clk* primitive



## DCO with Linear D-to-f

- models/dco\_lin.sv


```
// digital-to-frequency conversion (linear)
always @(in) begin
    freq = fcenter + Kdco*real'(in - `pow(2, Nbit-1));
end
real_to_xreal conn(.in(freq), .out(freq_xr));

// frequency-to-clock conversion
freq_to_clk #(.num_phase(1), .PN_foffset(PN_foffset),
               .PN_fcenter(PN_fcenter), .PN_dbc(PN_dbc))
freq2clk(.out(out), .in(freq_xr));

...
```
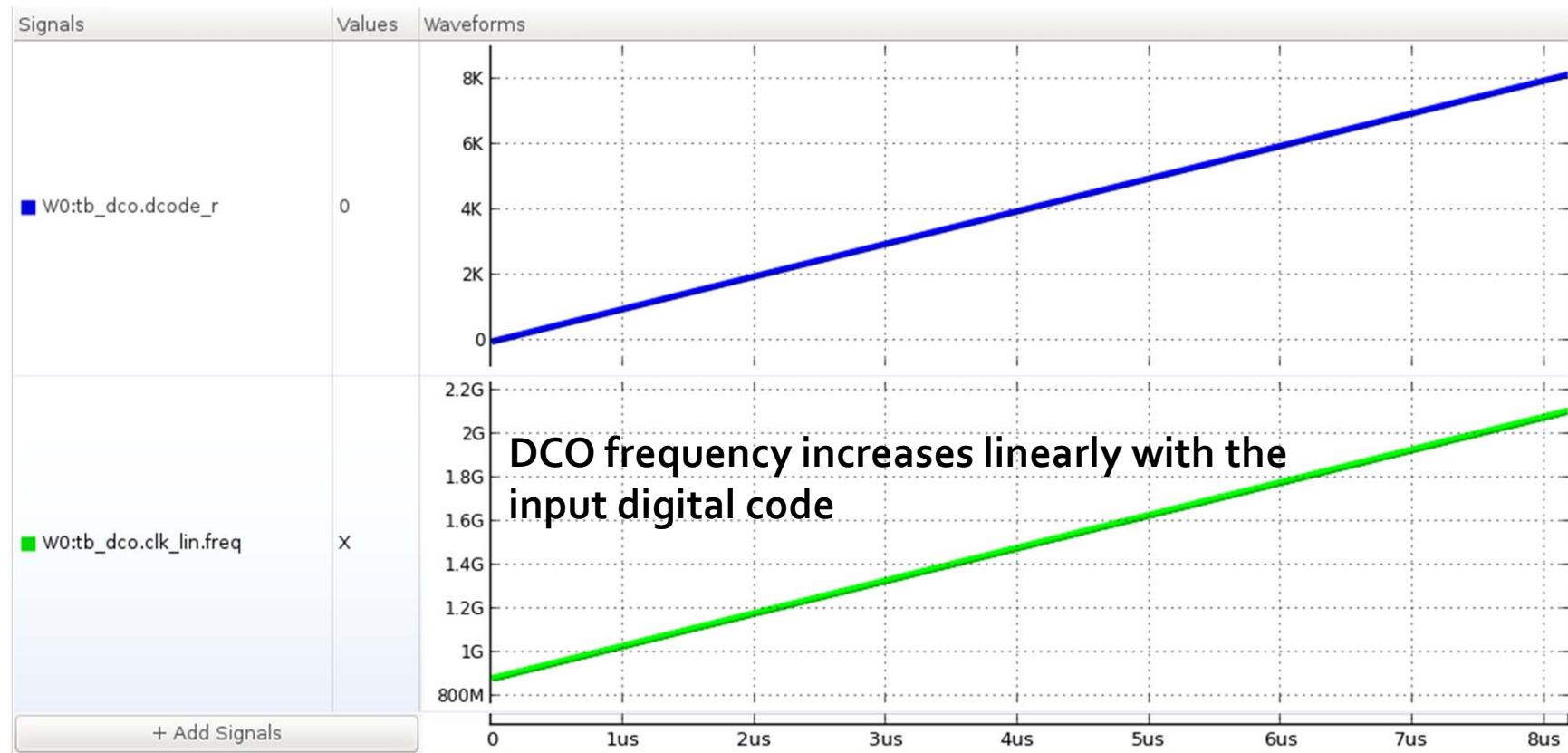
# Exercise


- Plot the D-to-f characteristic of the DCO
  - sim/tb\_dco\_lin





# One Caveat with Digital PLLs

- PVT dependencies of DCO and TDC characteristics often require calibration circuits and routines
- Complexity may become much higher than CP PLLs

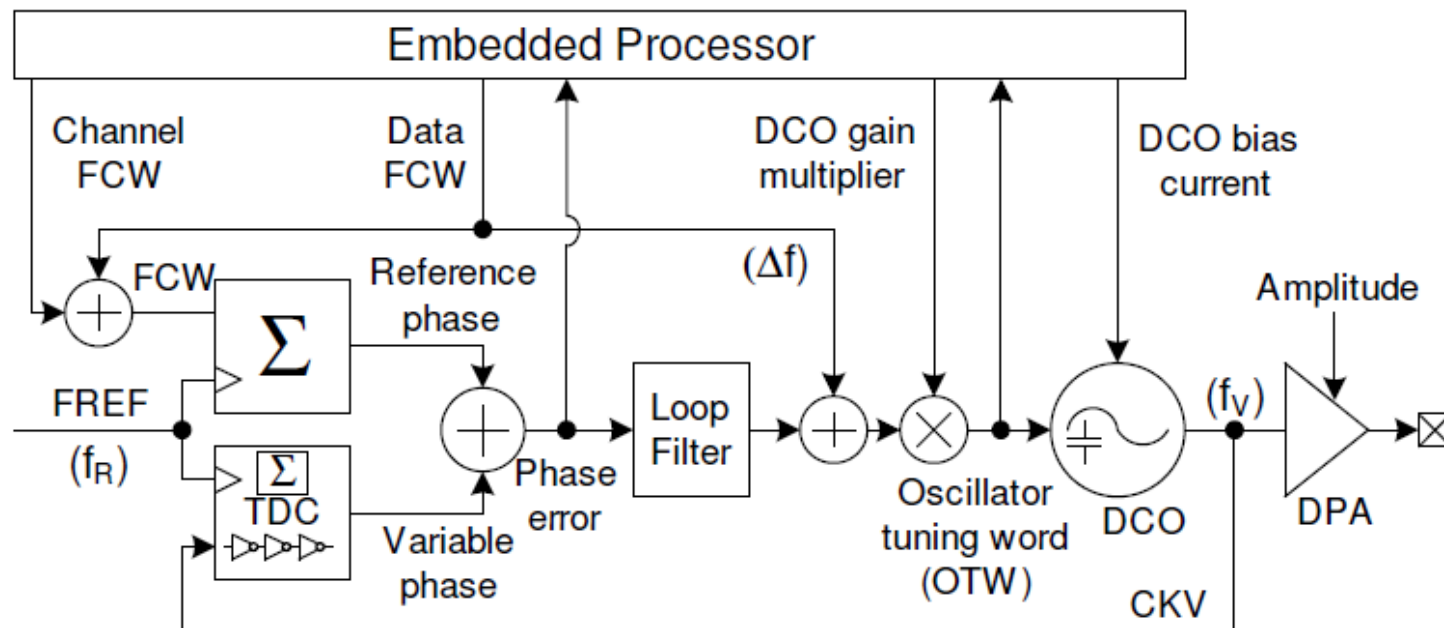

[Staszewski10]


# Self-Biased (Adaptive-BW) PLLs

- In analog PLLs, a common way to address PVT is to scale bandwidth with frequency [Maneatis 96]
  - Input frequency is the most reliable to set the BW with

$$\begin{aligned}
 I_{CP} &\propto I_{VCO} \\
 R_{CP} &\propto R_{VCO}
 \end{aligned}$$



↓
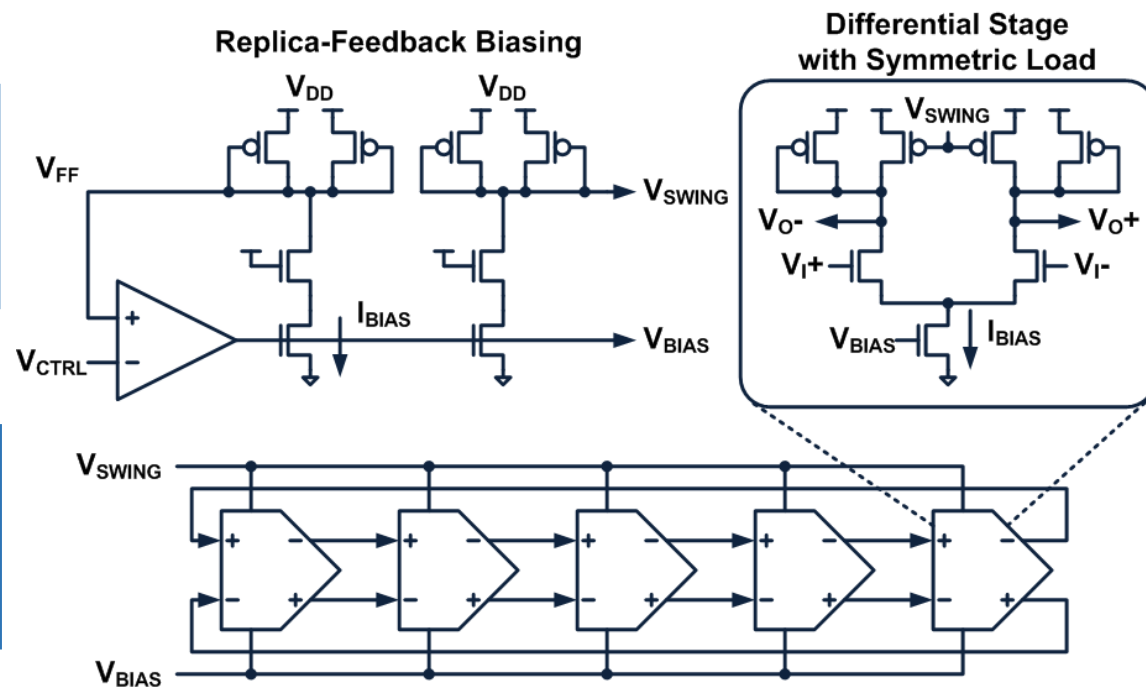
$$\begin{aligned}
 BW/f_{REF} &\sim \text{const.} \\
 \zeta &\sim \text{const.}
 \end{aligned}$$


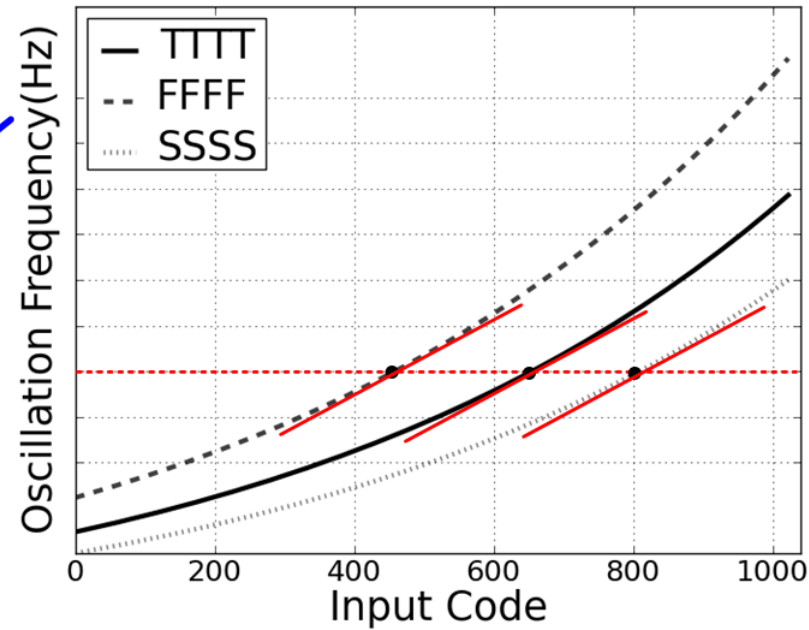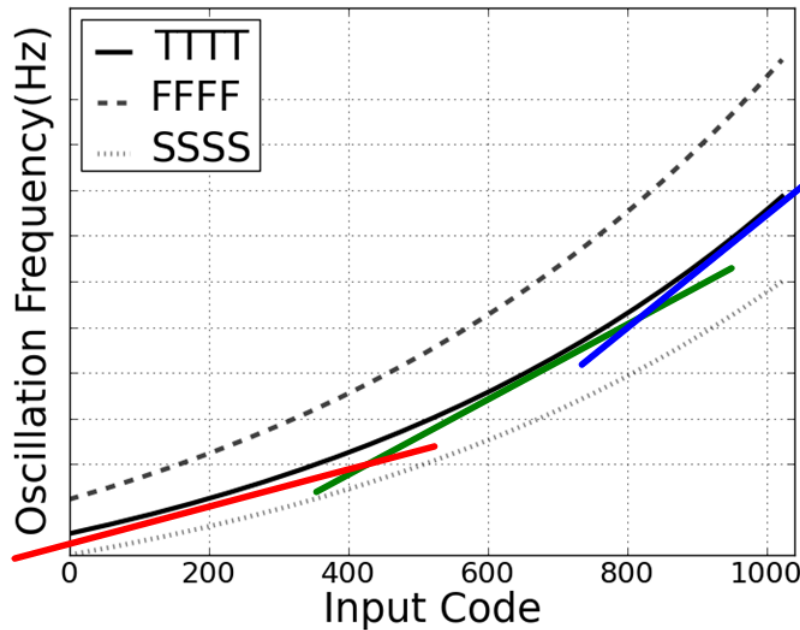
# Adaptive-Bandwidth Digital PLLs

- Equivalent adaptive-BW can be achieved by realizing an **exponential  $D$ - $f$  curve** for the DCO
  - $K_{\text{DCO}}$  scaling with the frequency (left)
  - $K_{\text{DCO}}$  constant over PVT at a given frequency (right)



## Exercise


- Fill the blank in dco\_exp.sv so that the DCO has:
  - 12-bit resolution ( $f=5\text{GHz}$  when  $D = 12'b1000\_0000\_0000$ )
  - Relative gain of  $0.004\%/step$

```
// digital-to-frequency conversion (exponential)
always @(in) begin
    // FILL BELOW TO DESCRIBE AN EXPONENTIAL
    // D-to-F CHARACTERISTIC
    // HINT: Use `pow(X, Y) to compute X^Y
    freq = ...;
end

real_to_xreal conn(.in(freq), .out(freq_xr));
```


# Results

- sim/tb\_dco\_all:

 

 
# Frequency Divider

- Synchronous dividers have best jitter but slow
- Asynchronous dividers (e.g. ripple carry counter) are simple but accumulate jitter through the long delay path




**Synchronous Divider**

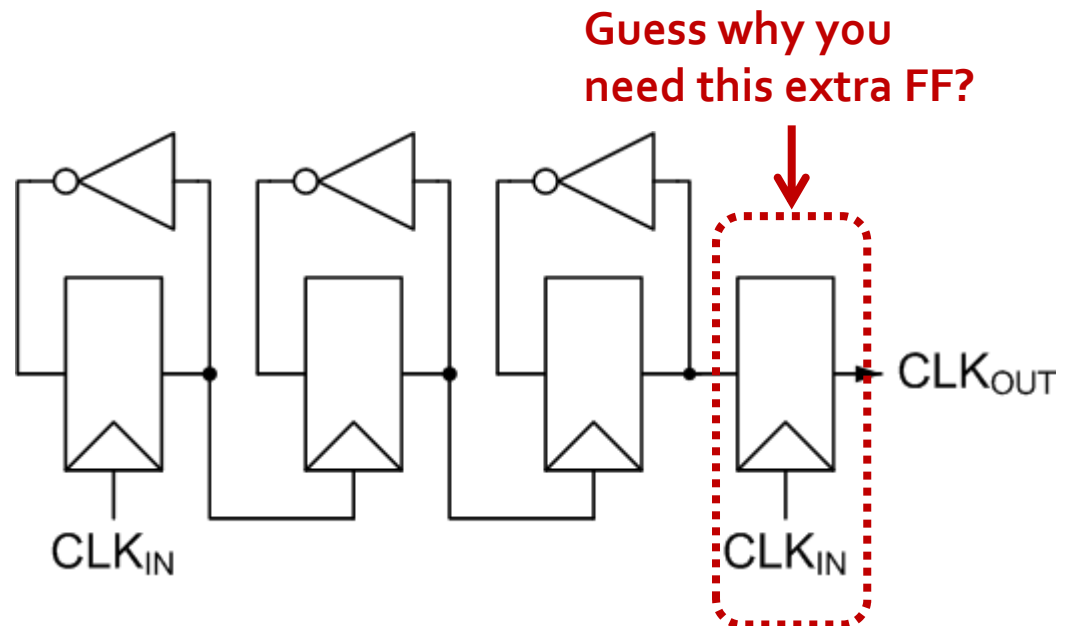

**Asynchronous Divider**
 
## Exercise

- Examine the two frequency divider models:
  - Synchronous divider: models/fdiv16\_sync.sv
  - Asynchronous divider: models/fdiv16\_async.sv
- Run the testbench in sim/tb\_fdiv16:



*What is the difference between the two divider outputs?*

## Exercise (cont.)

- Modify the asynchronous divider model so that its clock-to-Q delay is reduced
  - Add a retiming FF as shown in the previous slide
  - Answer: `sim/tb_fdiv16/answer/fdiv16_async_retimed.sv`

